

Photo Description



A person is using wires to connect a small light bulb to a battery. The light bulb is glowing bright, which means electricity is flowing through the wires. This shows how we can make a simple electric circuit.

Scientific Phenomena

This image demonstrates the Anchoring Phenomenon of electrical circuits and conductivity. The light bulb illuminates because electrical current flows from the battery through the conducting wires to the bulb and back to complete a closed circuit. The wires act as conductors, allowing electrons to move freely through the metal, while the battery provides the energy source (electrical potential difference) that drives this flow of electric current.

Core Science Concepts

1. Electric Circuits: Electricity needs a complete path (circuit) to flow from one end of a battery to the other end
2. Conductors: Some materials like metal wires allow electricity to flow through them easily
3. Energy Transfer: Batteries store energy that can be changed into light energy when connected properly
4. Cause and Effect: When we connect the circuit correctly, the bulb lights up; when we disconnect it, the light goes out

Pedagogical Tip:

Start with hands-on exploration before introducing vocabulary. Let students experiment with connecting batteries and bulbs first, then introduce the scientific terms after they've observed the phenomena.

UDL Suggestions:

Provide multiple ways for students to demonstrate understanding: drawing circuits, building physical models, acting out electron flow with their bodies, or using digital circuit simulators for different learning preferences.

Zoom In / Zoom Out

1. Zoom In: Inside the metal wires, tiny particles called electrons are moving very fast from one end to the other, like cars on a highway, carrying energy to make the bulb glow
2. Zoom Out: This same principle powers our homes, schools, and cities through much larger electrical systems that bring electricity from power plants through power lines to light up entire communities

Discussion Questions

1. What do you think would happen if we removed one of the wires? (Bloom's: Predict | DOK: 2)
2. Why do you think the bulb lights up when connected to the battery? (Bloom's: Analyze | DOK: 2)

3. What other materials could we test to see if electricity flows through them? (Bloom's: Create | DOK: 3)
4. How is this simple circuit similar to the lights in our classroom? (Bloom's: Compare | DOK: 2)

Potential Student Misconceptions

1. Misconception: "Electricity gets used up as it travels through the circuit"
Clarification: Electricity flows in a complete loop - the same amount that leaves the battery returns to it
2. Misconception: "The battery makes electricity"
Clarification: The battery stores energy and pushes electricity through the circuit, like a pump pushes water through pipes
3. Misconception: "Electricity only flows one way through wires"
Clarification: Electricity flows in a complete circle from one end of the battery, through the circuit, and back to the other end

Cross-Curricular Ideas

1. Math Connection - Counting & Patterns: Have students count how many wires, batteries, and bulbs are needed to make a circuit work. Create patterns with different colored wires and predict what comes next in the sequence.
2. ELA Connection - Procedural Writing: Ask students to draw pictures and write simple sentences describing the steps to build a circuit: "First, we get a battery. Next, we connect a wire. Then, the bulb lights up." This develops sequencing skills and technical vocabulary.
3. Art Connection - Circuit Design: Students can create colorful circuit diagrams using markers, string, and stickers to show how electricity flows. They can design their own "circuits" on paper and label the parts with pictures and words.
4. Social Studies Connection - Community Helpers: Discuss how electricians use circuits to bring lights and power to our homes, schools, and hospitals. Students can learn that electricians help keep our communities safe and bright.

STEM Career Connection

1. Electrician: An electrician is a person who installs and fixes electrical wires and circuits in buildings like homes and schools. They make sure lights work, outlets are safe, and electricity reaches everywhere it needs to go. They use tools to connect wires and test circuits to keep people safe. Average Annual Salary: \$56,900
2. Electrical Engineer: An electrical engineer designs and invents new things that use electricity, like light bulbs, computers, phones, and toys. They solve problems by figuring out how to make electricity work better and safer. They draw plans and test their ideas before things are built. Average Annual Salary: \$104,000
3. Science Teacher: A science teacher helps students like you learn about circuits, electricity, and how things work. They do fun experiments and answer questions to help students discover and understand science. They make learning exciting and safe! Average Annual Salary: \$62,000

NGSS Connections

- Performance Expectation: K-PS3-1 - Make observations to determine the effect of sunlight on Earth's surface
- Disciplinary Core Ideas: PS3.A - Energy and Matter
- Crosscutting Concepts: Cause and Effect and Energy and Matter

Science Vocabulary

- * Circuit: A complete path that electricity can follow in a loop
- * Conductor: A material that lets electricity flow through it easily
- * Battery: A device that stores energy and can push electricity through wires
- * Current: The flow of electricity through a wire or circuit
- * Energy: The power needed to make things work or change

External Resources

Children's Books:

- Switch On, Switch Off by Melvin Berger
- The Magic School Bus and the Electric Field Trip by Joanna Cole
- Oscar and the Bird: A Book About Electricity by Geoff Waring